



# United International University

Department of Computer Science and Engineering


Course Code: EEE 2113 | Course name: Electrical Circuit

SUMMER 2021 | FINAL Examination | 25 marks |

Exam Time : 1 hour 15 minutes, Upload Time : 15 minutes


There are five (5) questions here. You have to answer all of them.

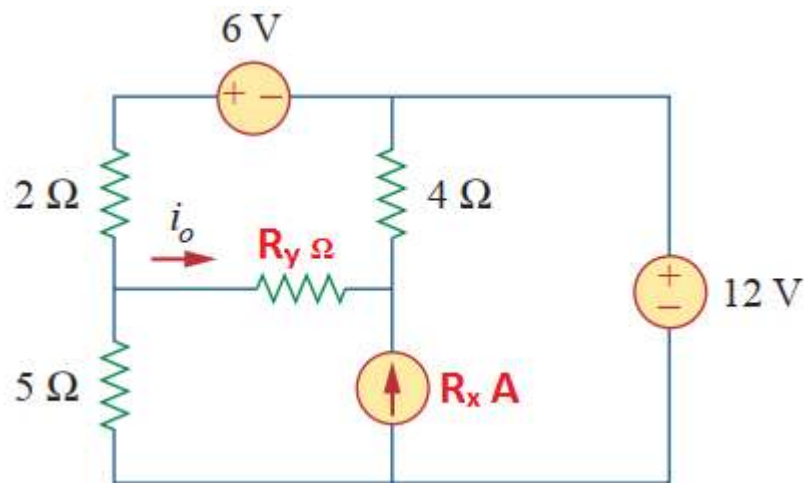1. Use **Superposition theorem** to find  $i_o$  in the following circuit.




Here,  $R_x = (\text{last two digits of you ID} \% 20) + 10$   
 $R_y = (\text{last two digits of your ID} \% 10) + 2$

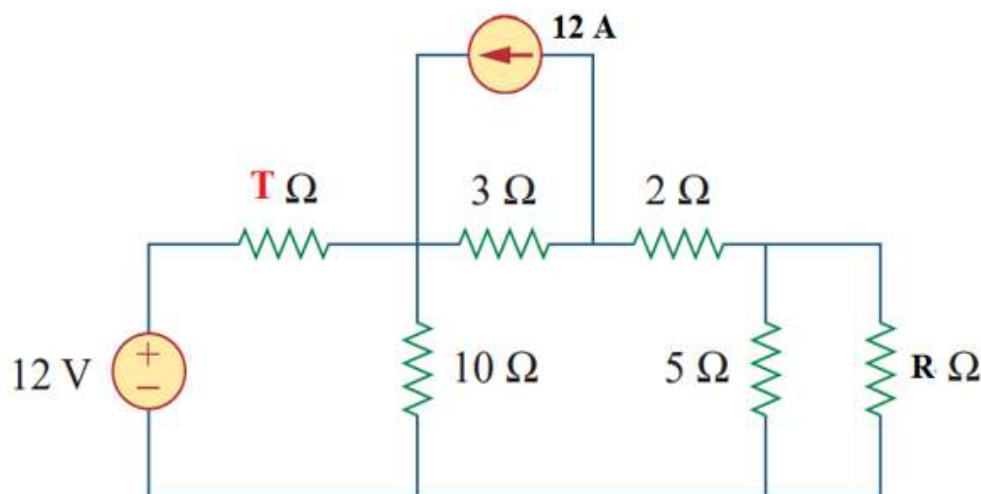2. In the following figure,  $T = ((5 * \text{last digit of your class ID}) \% 9) + 1$ . Determine the maximum power that can be delivered to the variable resistor  $R$  in the following circuit.



3. Find out the Norton Equivalent circuit to the left of the terminals a-b in the following circuit, and use the simplified circuit to find out the value of  $i$ .

5

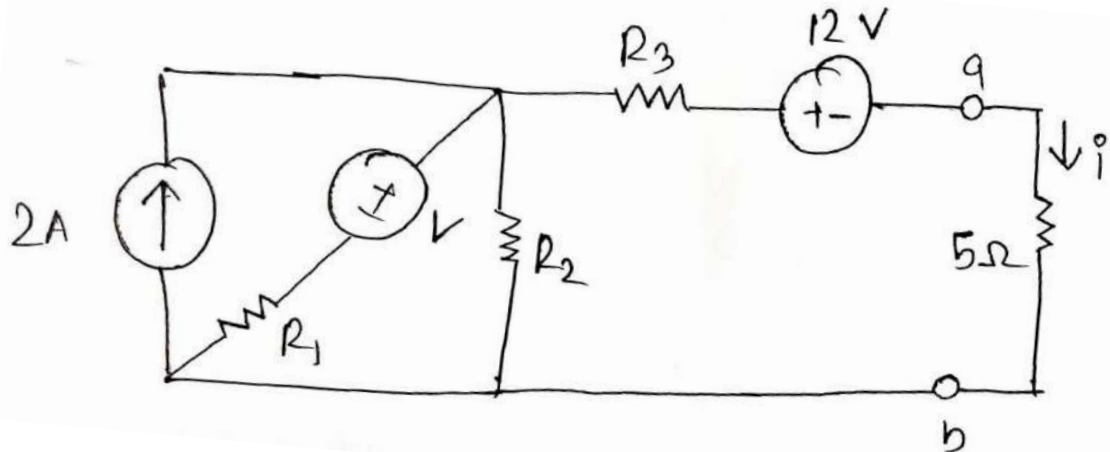


1.  $R_1 = (1 + \text{Last Digit of your Student ID}) \text{ Ohms}$
2.  $R_2 = (2 + \text{Second Last digit of your Student ID}) \text{ Ohms}$
3.  $R_3 = (3 + \text{Third Last Digit of your Student ID}) \text{ Ohms}$
4.  $V = (\text{Last Three Digits of your Student ID}) \text{ Volts}$

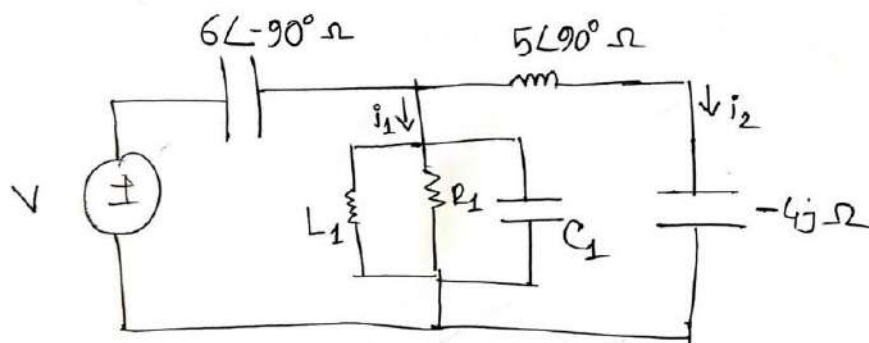
4. In the following circuit, calculate the equivalent impedance of the  $L_1$ ,  $R_1$ , and  $C_1$  combination in the circuit. Also use current/voltage division to find out  $i_1$  and  $i_2$ .

5

- Here,
- $C_1 = (1 + \text{Last Digit of your Student ID}) \text{ Farads}$
- $L_1 = (1 + \text{Second Last digit of your Student ID}) \text{ Henry}$
- $R_1 = (1 + \text{Third Last Digit of your Student ID}) \text{ Ohms}$
- $V = (\text{Last Three Digits of your Student ID}) * \sin(10t + 30) \text{ Volts}$



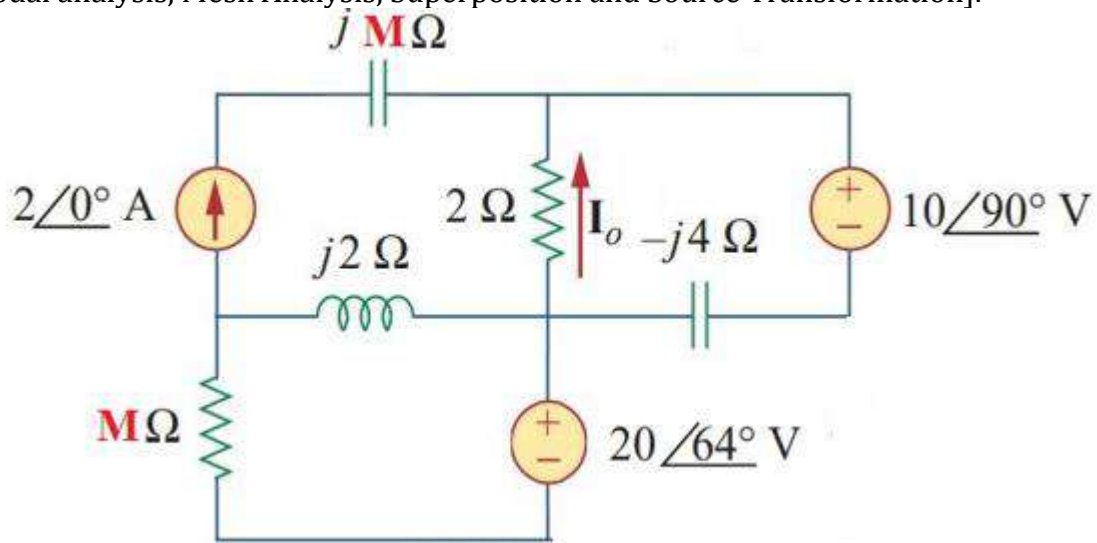5. In the following figure,  $M = ((3 * \text{Sum of Last two digit of your Class ID}) \% 7) + 3$ . Find out  $I_o$  using any of your desired method among the taught circuit analysis methods [Nodal analysis, Mesh Analysis, Superposition and Source Transformation].



**Any examinee found adopting unfair means will be expelled from the trimester / program as per UIU disciplinary rules**

