



# United International University

Department of Computer Science and Engineering


Course Code: EEE 2113 | Course name: Electrical Circuit

Summer 2021 | MID Examination | 20 marks | 60min

**There are five (4) questions here. Answer all of them**

1. In the following resistor, value of each resistance is  $R \Omega$ . ( $R$  = First digit of your birthdate + Last digit of Your Class ID + 2). Find out the  $R_{eq}$  at Terminal AB (Marked in the Figure).


[5]

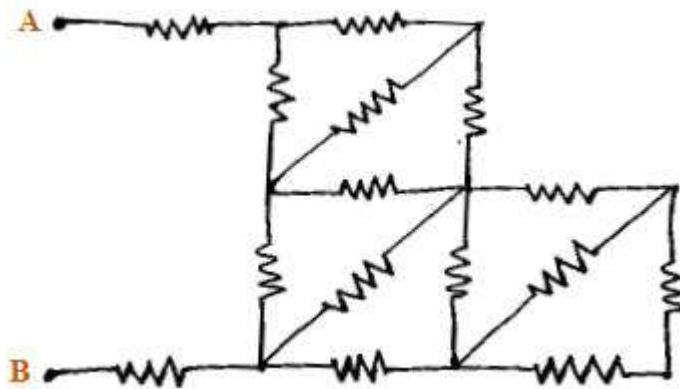

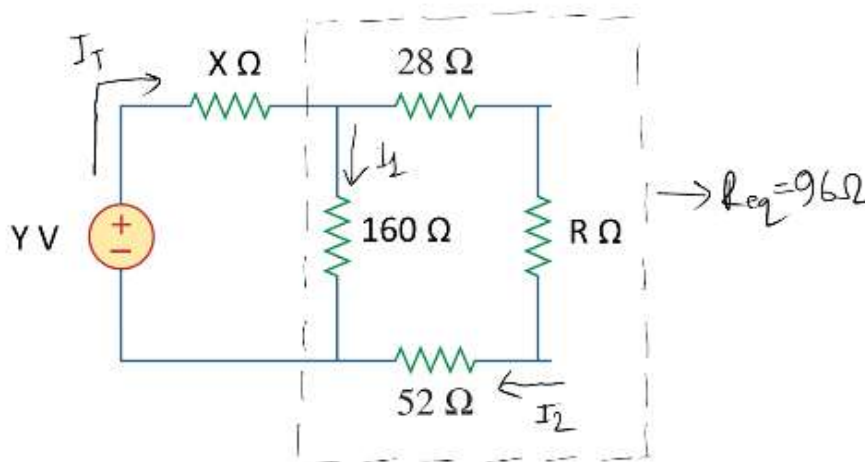2. Given that:

[5]

- The equivalent resistance of the portion that has been marked with dotted lines in the following Circuit,  $R_{eq}$  is  $96 \Omega$ .
- The value of  $Y$  is the last three digits of your student ID
- The value of  $X$  is the day-value of your birth date (i.e., if your birthday is dd-mm-yyyy, then the Value of  $X$  is dd).




Find the following:

- The voltage through the  $X \Omega$  resistor
- The current  $I_1$
- The resistance  $R$
- The currents  $I_1$  and  $I_2$


3. In the following figure,  $T = (40 / \text{your birthdate})$  Amp and  $R = (\text{Last Digit of your ID no} + 5) \Omega$ . Find out the value of mesh Currents  $i_1, i_2, i_3$  and  $i_4$ .

[5]

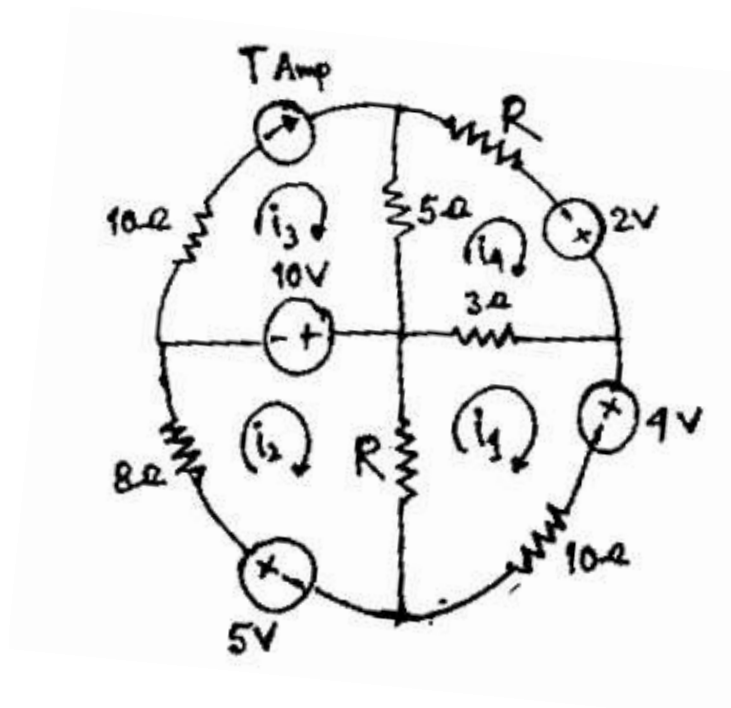

4. Find the node voltages for the following circuit. Also, find out the power at resistor  $4 \Omega$ .

[5]

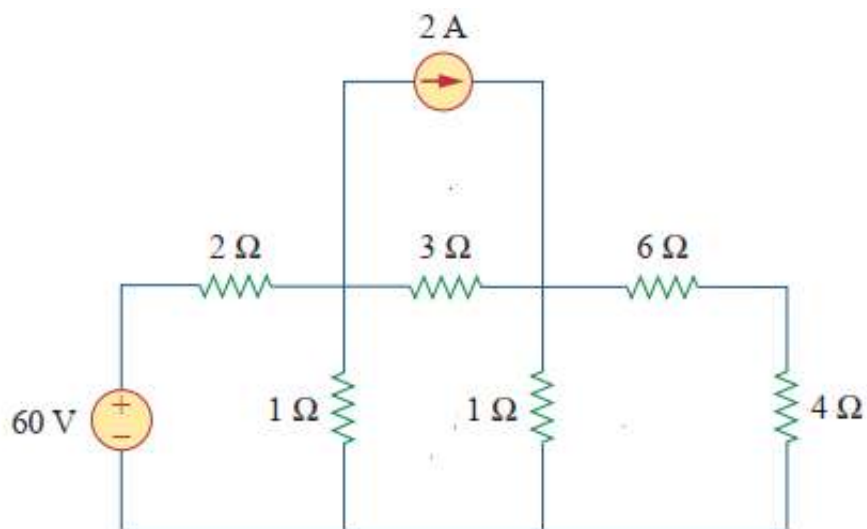

**Any examinee found adopting unfair means would be expelled from the trimester / program as per UIU disciplinary rules**