



# United International University

Department of Computer Science and Engineering

Course Code: EEE 2113 | Course name: Electrical Circuit

Fall 2020 | MID Examination | 20 marks | 60min

There are five (5) questions here. Question 1, 2 & 3 are mandatory. Answer any one from question 4 & 5.

## Data Generation for example ID - 011xxyyzz

Last 6 digits will be used as data	011	$R_{xx}$	$R_{yy}$	$R_{zz}$
Example ID	011	xx	yy	zz
Your ID	011			

1. Obtain the equivalent resistance at the terminals a-b. All resistors have a value of  $R_{yy} \Omega$ . [5]

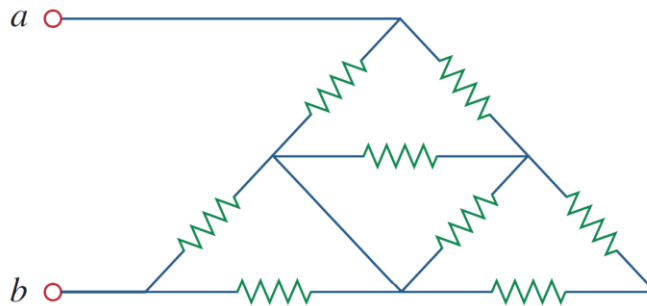


Figure for Q-1

2. Find  $V_1, V_2, I_1, I_2, I_3$  &  $I_4$  in the following circuit using voltage and current division rules. [5]

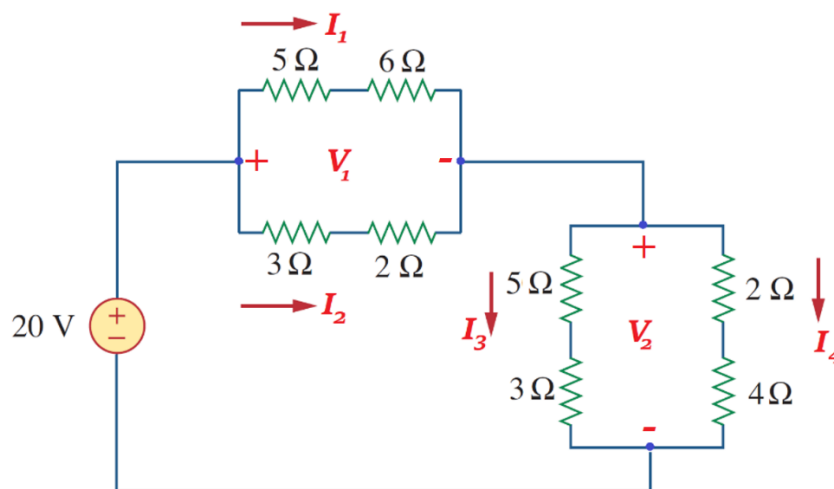


Figure for Q-2

3. Power consumed by a  $10\ \Omega$  resistor is given by, [5]

$$p(t) = 1000\cos^2(R_{xx}\pi t)\ W$$

- Derive the expression of current  $i(t)$  through this resistor.
- Derive an expression for charge  $q(t)$ .
- Calculate the amount of charge flown through the resistor within  $70\ ms$ .
- Write down the expression of voltage  $v(t)$  across the resistor.

4. Use mesh analysis method to find  $v_0$  in the following circuit. [5]

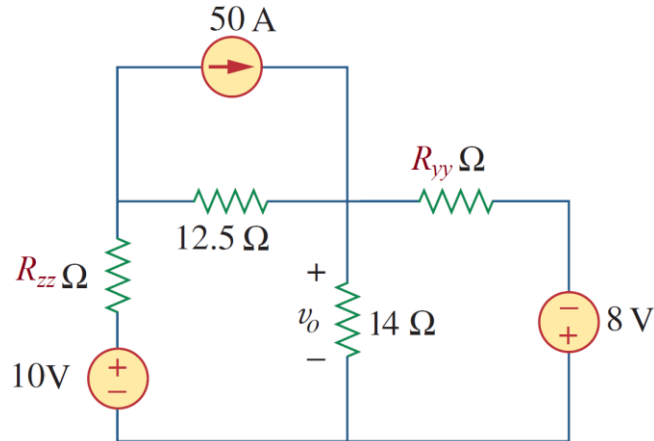


Figure for Q-4

5. Use node analysis method to obtain  $v_0$  in the following circuit. [5]

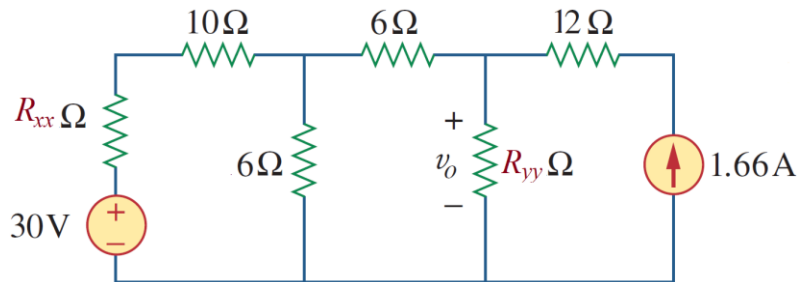


Figure for Q-5

**Any examinee found adopting unfair means will be expelled from the trimester / program as per UIU disciplinary rules**