



# United International University

Department of Computer Science and Engineering

Course Code: EEE 2113 | Course name: Electrical Circuit

SPRING 2022 | FINAL Examination | 40 marks | 2 hours

There are five (5) questions here. You have to answer all of them.

1.

8

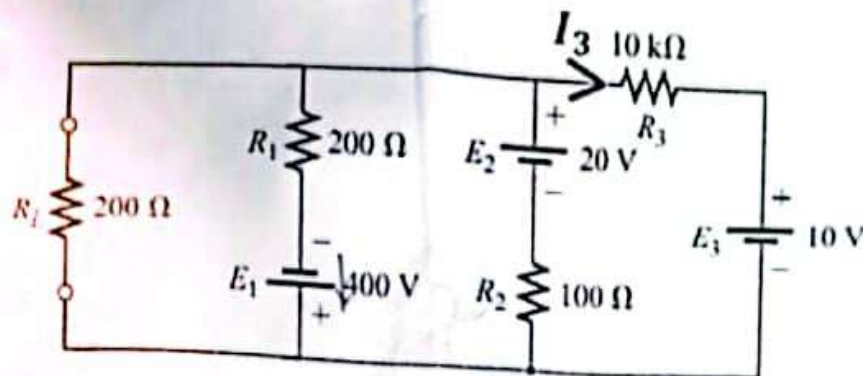


Fig. Q1 for Question 1

- Determine the voltage across the load resistance ( $R_L$ ), using source transformation theorem for the above circuit in Fig. Q1.
- Determine the current  $I_3$  using superposition theorem for the above circuit in Fig. Q1.

2.

8

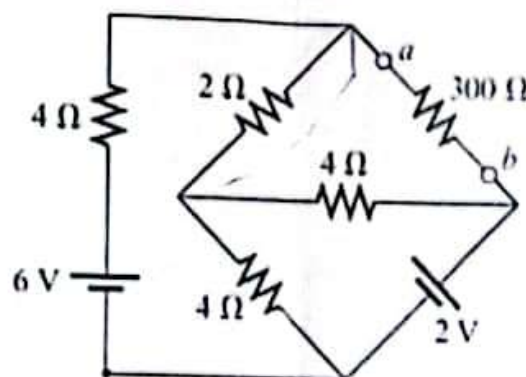


Fig. Q2 for Question 2

For the above circuit shown in Fig. Q2, answer the following questions:

- Determine the Norton Equivalent circuit at terminal a-b.
- Determine the current through the  $300\Omega$  using the Norton equivalent circuit determined in (a).

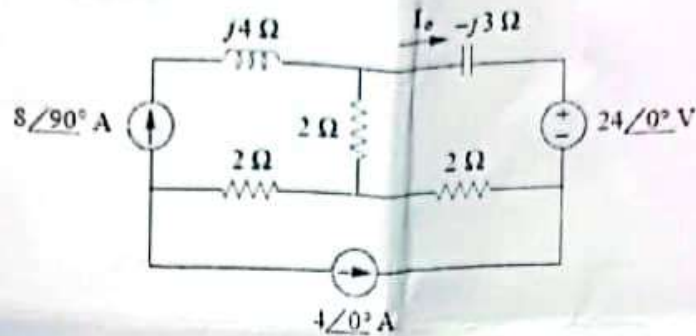


Fig. Q3 for Question 3

Find  $I_o$  in the following circuit shown in Fig. Q3 using superposition theorem.

8

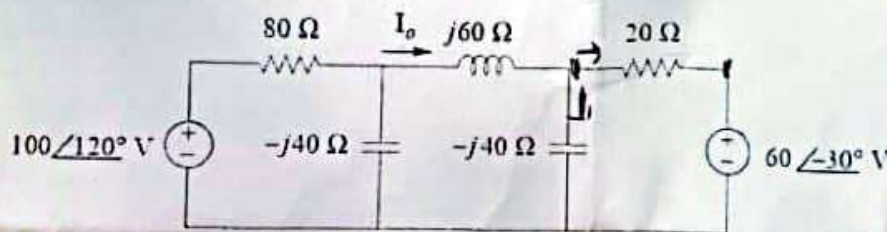


Fig. Q4 for Question 4

- (a) Find  $I_o$  using **nodal analysis** method for the above circuit shown in Fig. Q4.  
 (b) Also find the **voltage** across the  $20\ \Omega$  resistor for the above circuit shown in Fig. Q4.

8



Fig. Q5 for Question 5

- (a) Find the Thevenin equivalent circuit for the network external to the resistor  $R$  in the above circuit shown in Fig. Q5.  
 (b) Find the **value** of  $R$  for maximum power absorption and also calculate the amount of maximum absorbed power by  $R$  Fig. Q5.

Any examinee found adopting unfair means will be expelled from the trimester / program as per UIU disciplinary rules