




United International University (UIU)
Dept. of Computer Science & Engineering (CSE)
Mid-Term Examination

EEE 2123: Electronics, Trimester: Fall 2021
Total Marks: 30, Duration: 1 hour 45 minutes

1. (a) A current of 1 mA flows through a silicon diode along $p \rightarrow n$ direction due to 1 V biasing voltage. The reverse saturation current and ideality factor of the diode are 10^{-4} nA and unity respectively. [6]
- CO-1
- Comment on the biasing type (forward or reverse) of the diode.
 - Calculate the thermal voltage.
 - Determine the operating temperature of the diode.
 - What will be the new saturation current if the temperature is reduced by 20°C ?

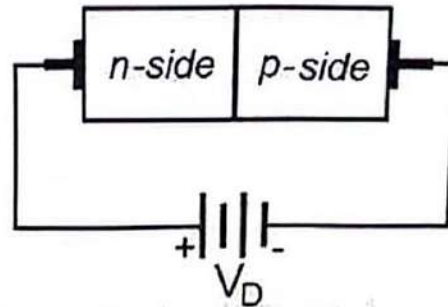(b) Find the biasing of the following diode for given cases. Note that, $V_{ON} = 2\text{ V}$ and $V_{br} = 5\text{ V}$. Also comment on the approximate value of current in each case.

- $V_D = 1\text{ V}$
- $V_D = -1\text{ V}$
- $V_D = 10\text{ V}$
- $V_D = -10\text{ V}$



2. The input voltage v_i to the following rectifier circuit is a sine-wave with 20 V amplitude. [8]

CO-2


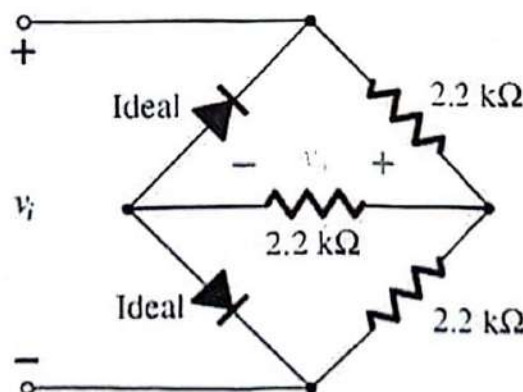


Figure for Q-2

- Derive the expression of v_o and sketch it mentioning the peak values in the curve.
- What is the maximum value of v_o ?
- What is the average value of v_i & v_o ?
- Calculate PIV of any diode.
- Based on the calculated PIV in Q-2(d), comment on the probable breakdown voltage of the diodes.


3. Find I_{o1} & I_{o2} , V_{o1} & V_{o2} in the following circuit. You must draw the equivalent circuit. [6]

CO-2

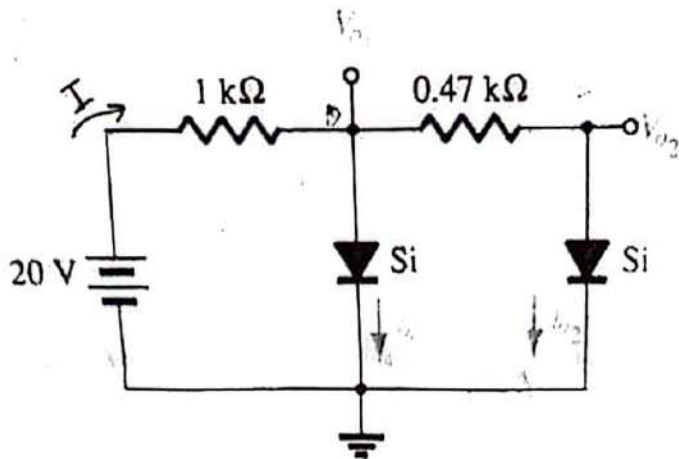


4. Derive the expressions of v_o , v_R and i_R for the given v_i and sketch them. [6]

CO-2

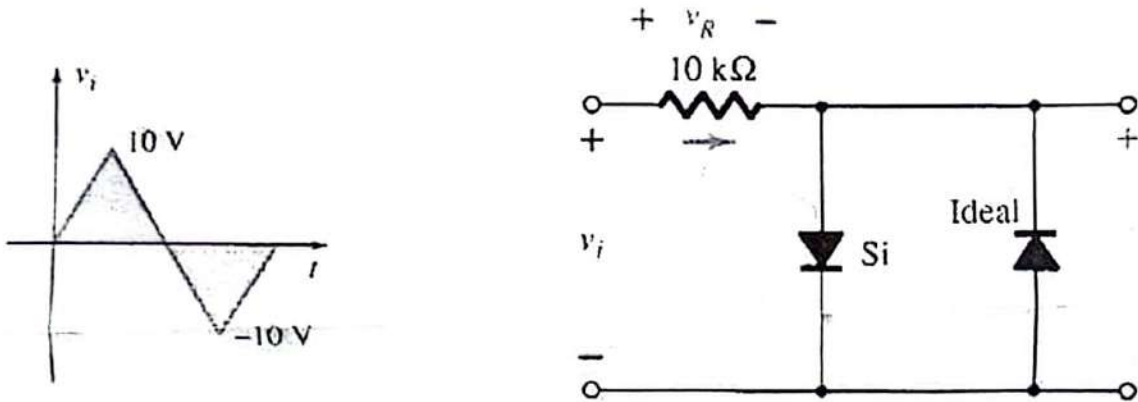

5. Sketch v_o for the following circuit mentioning peak values appropriately. [4]

CO-2

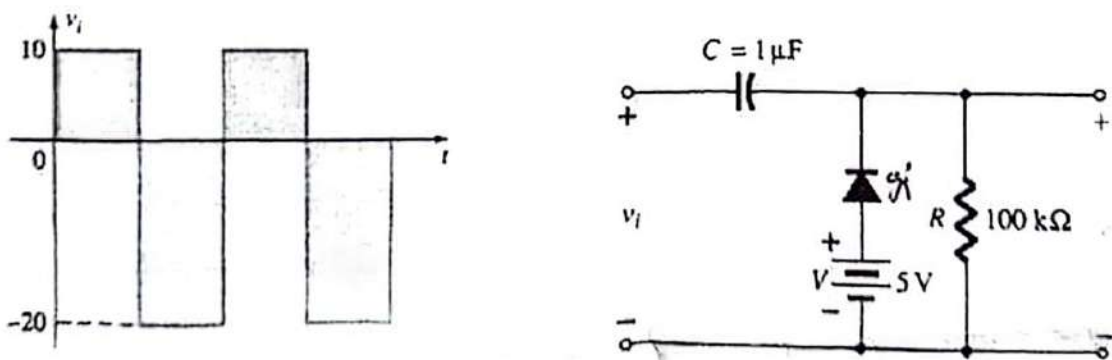

COs	Description
CO-1	Describe the operating principle of semiconductor diodes and transistors using knowledge of basic semiconductor physics
CO-2	Analyze small analog electronic circuits by applying simple lumped circuit models of diodes and transistors