



United International University (UIU)
Dept. of Computer Science & Engineering (CSE)
Mid-Term Exam: Trimester: Summer 2023

Course Code: EEE 2123; Course Title: Electronics
Total Marks: 30; Duration: 1 hour 45 minute

Any examinee found adopting unfair means would be expelled from the trimester/ program as per UIU disciplinary rules.

1. Suppose a diode with following specifications is operating at 40°C .

$$I_s = 5 \text{ nA}, n = 2, V_{on} = 1.05 \text{ V} \text{ \& } |V_{br}| = 4 \text{ V}$$




For the current listed below, fill out the following table: [4]


Case	Current (I_D)	Biasing type	ON/OFF/Breakdown	V_D
1	9 A (a→b)			
2	7 mA (a→b)			
3	5 nA (b→a)			
4	100 nA (b→a)			

Also draw the I/V curve of the diode and **locate the points (I_D, V_D)** accordingly. [2]

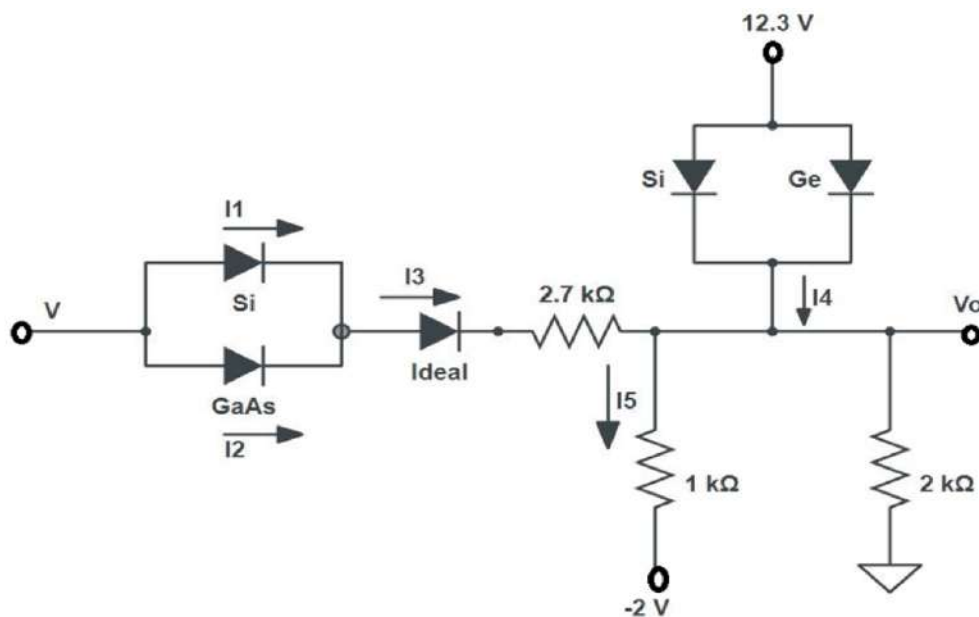
2. (a) Find the currents I_1, I_2, I_4, I_5 & voltages V_o, V such that $I_3 = 1 \text{ mA}$. [7]



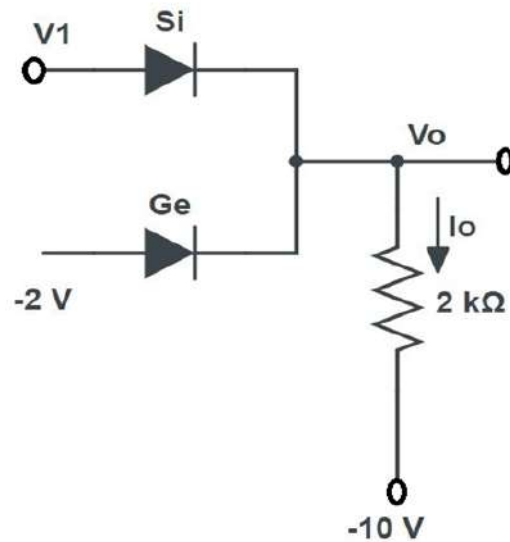(b) Can any value of V_1 turn both the diodes on? If so, find voltage V_o and current I_o . [4]




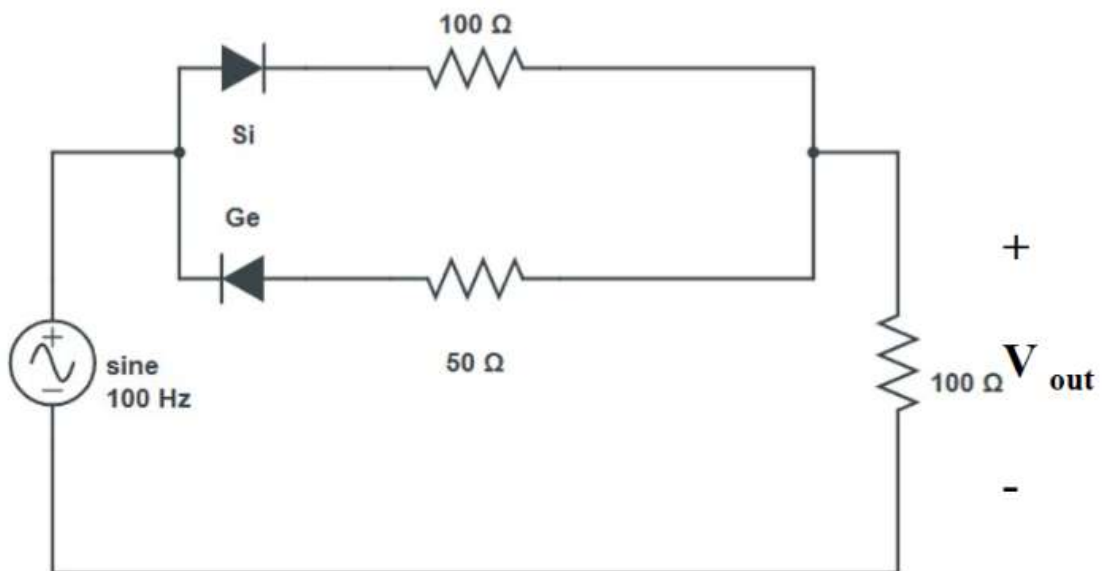3. Consider the input voltage for the following circuit to be a sine wave with an amplitude of 10V and frequency of 100 Hz.



- 1) Find the time at which the Si diode starts conduction. [2]
- 2) Draw the output waveform of V_{out} with proper label values. [2]
- 3) Can this circuit be considered as a rectifier? Justify your answer. [1]

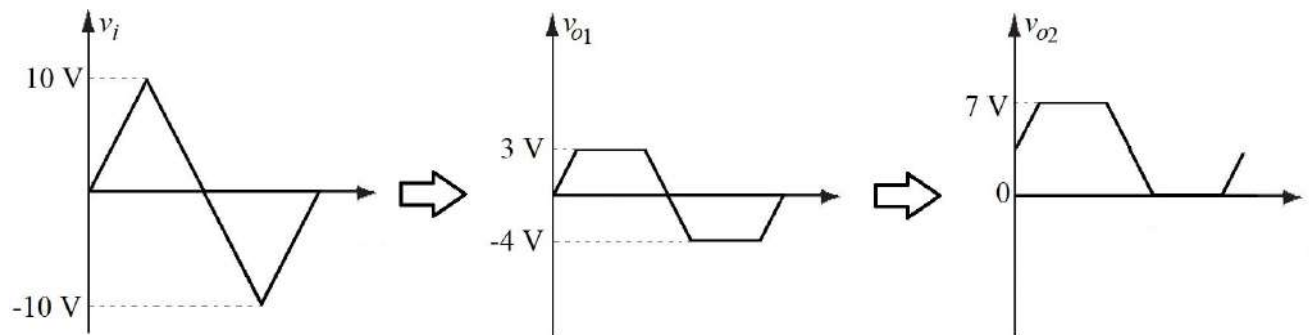4. Design a circuit that can generate the output v_{o1} from given v_i . Design another circuit that takes v_{o1} as input and gives v_{o2} as output. Assume all diodes to be Ge throughout your design. [3+2]



5. For the following circuit, consider input v_i to be a rectangular voltage pulse with 10V peak. Derive the expression of v_o and sketch it with proper labeling. [3]

