





United International University (UIU)
 Dept. of Computer Science & Engineering (CSE)
Midterm Exam : Trimester: Fall - 2017

Course: CSE 113 Electrical Circuits,
 Marks: 30, Time: 1 hour 45 minutes

Figures in the right-hand margin indicate full marks.

Answer Any Three out of the Four Question Sets

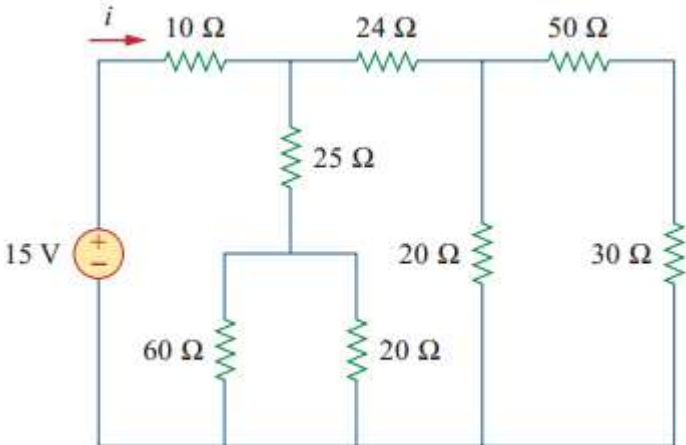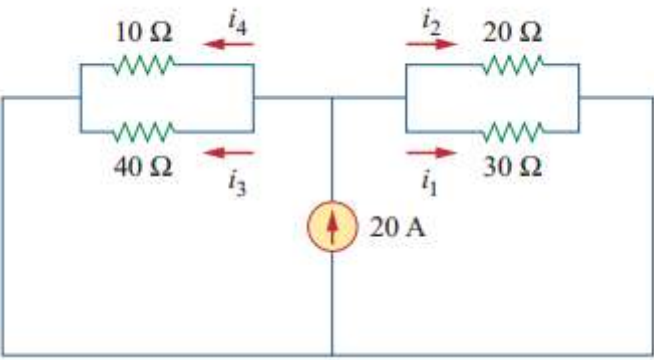2.	<p>a) Determine i in the following circuit.</p> 	5
	<p>b) Find i_1, i_2, i_3, i_4 for the following circuit.</p> 	5

2.	a)		4
	b)	$ \begin{array}{c} + \\ V_0 \\ - \end{array} $	6
3.	a)		6

	b)		4
--	----	--	----------

4.	a)		4
	b)		6