



United International University (UIU)
Dept. of Computer Science & Engineering (CSE)
Final Exam, Trimester: Spring 2024

Course Code: CSE 113/EEE 2113; Course Title: Electrical Circuits

Total Marks: 40; Duration: 2 hours

Any examinee found adopting unfair means would be expelled from the trimester/ program as per UIU disciplinary rules.

Question 1: Answer all the questions.

(10 Marks)

Use the superposition theorem to **determine** the value of V_x for the circuit shown in **Figure 1**. [8+2]
Also, the 8-ohm resistor absorbs power from both independent sources. **Analyze** the circuit and **determine** which independent source in this circuit supplies most of the power to the 8-ohm resistor. **CO3**

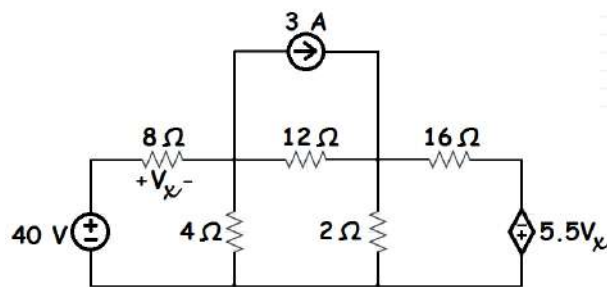


Figure 1

Question 2: Answer all the questions.

(10 Marks)

For the circuit shown in **Figure 2**, answer the following questions:

- Determine** the **Thevenin equivalent** circuit at the **a-b** terminal. [4+3+3]
- Suppose, your friend suggests that if you connect a **20V-40W** bulb across **a-b** terminal, then you will get maximum bulb intensity. Is he right? If not, then **calculate** the resistance of the bulb that would get maximum intensity. **CO3**
- Determine** the maximum power delivered to the bulb that would be connected across the **a-b** terminal.

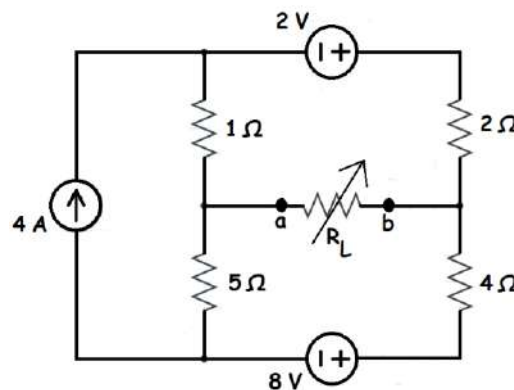


Figure 2

Question 3: Answer all the questions**(10 Marks)**

For the circuit shown in **Figure 3**, where $v_g(t) = 247.49 \cos(1000t + \pi/4)$

[3+3+

i) **Determine** the total impedance of the circuit.


2+2]

ii) **Determine** the current through the 100Ω resistor using the current division rule.

CO4

iii) **Determine** the voltage $V_{ab}(t)$ using VDR.


iv) **Determine** by how much degree the voltage, $V_{ab}(t)$ is leading the source voltage, $v_g(t)$.

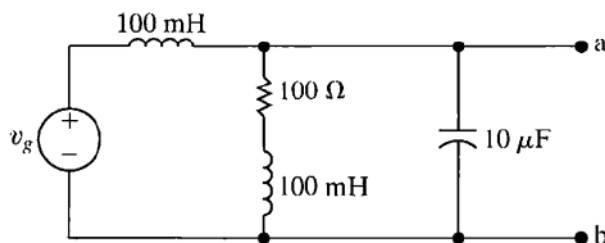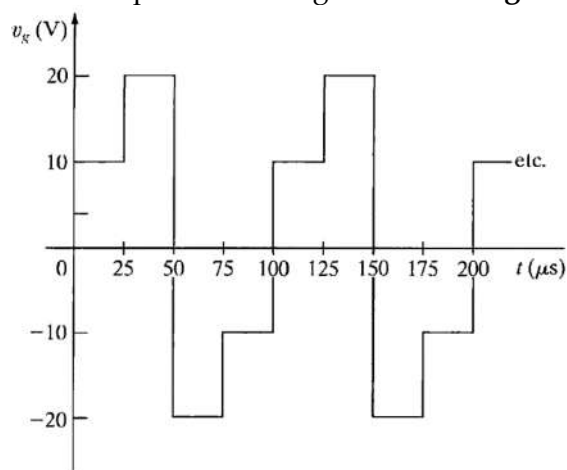**Figure 3****Question 4: Answer all the questions.****(10 Marks)**


Answer the following questions for the circuit shown in **Figure 4 (a-b)**:

[5+5]

i) **Calculate** the rms value of the periodic voltage shown in **Figure 4a**.

CO4**Figure 4a**

ii) Now, **use** this rms value as the maximum amplitude of the sinusoidal voltage source in the circuit shown in **Figure 4b**. **Determine** $I_0(t)$ and average real power absorbed by the 2-ohm resistor in the circuit. The angular frequency is 100 rad/s in the circuit.

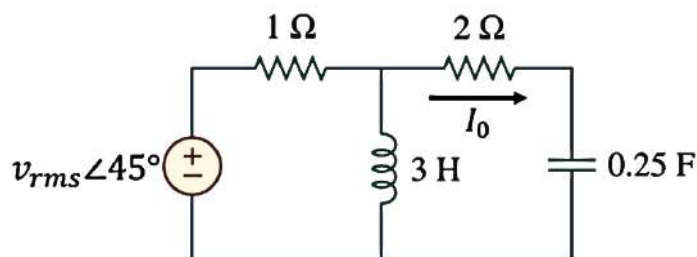**Figure 4b**