





United International University (UIU)
Dept. of Computer Science & Engineering (CSE)
Final Exam, Trimester: Fall 2023

Course Code: CSE 113/EEE 2113; **Course Title:** Electrical Circuits

Total Marks: 40; **Duration:** 2 hours

Any examinee found adopting unfair means would be expelled from the trimester/ program as per UIU disciplinary rules.

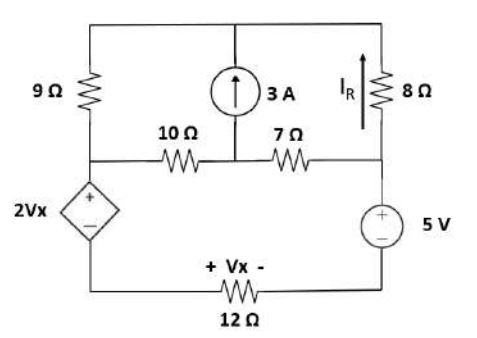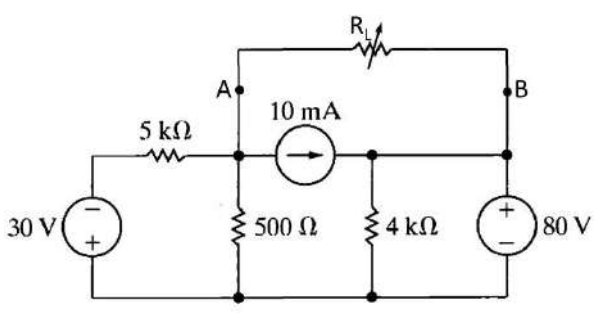Question 1: Answer all the questions.		(10 Marks)
<p>Answer the following questions for the circuit shown in Figure 1:</p> <p>i) Draw the circuit with the Independent Current Source Turned Off. ii) Draw the circuit with the Independent Voltage Source Turned Off. iii) Apply the Superposition Theorem, and find the value of I_R.</p>		[2+2+6]
 <p style="text-align: center;">Figure 1.</p>		
Question 2: Answer all the questions.		(10 Marks)
<p>For the circuit shown in Figure 2, answer the following questions:</p> <p>i) Determine the Thevenin equivalent circuit at the A-B terminal.</p> <p>ii) For any value of R_L, what will be the maximum power delivered to this resistance?</p> <p>iii) If $R_L=1k\Omega$, then would maximum power be achieved? If not, then what should you do to achieve maximum power?</p>		[6+2+2]
 <p style="text-align: center;">Figure 2.</p>		
Question 3: Answer all the questions		(10 Marks)
<p>Answer the following questions for the circuit shown in Figure 3:</p> <p>i) Determine Z_T. ii) Current, I. iii) Find the currents through 4Ω and 3Ω resistors.</p> <p>iv) Is the source voltage or the current, I leading in this circuit?</p>		[3+2+3+2]

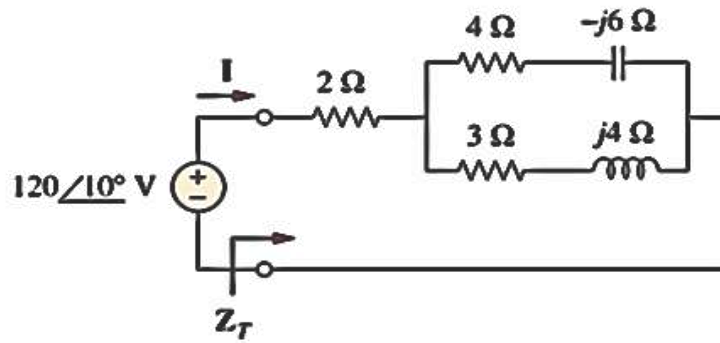


Figure 3.

Question 4: Answer all the questions.

(10 Marks)

For the circuit shown in **Figure 4a**, determine I_m if the rms value of such current is 5A. Now, determine i_o and average real power absorbed by a 3-ohm resistor using **CDR** in the circuit shown in **Figure 4b** if the angular frequency is 100 rad/s in the circuit.

[6+2+2]

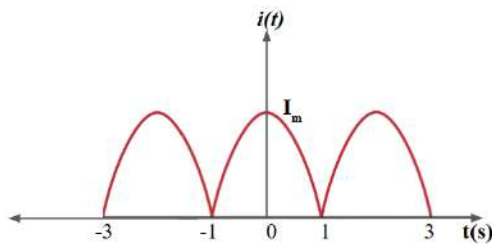


Figure 4a.

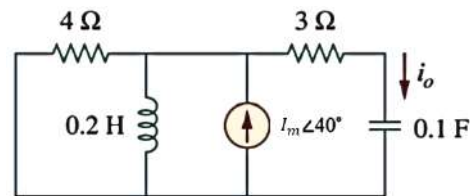


Figure 4b.