




United International University
Department of Computer Science and Engineering
EEE 2123: Electronics

Mid-Term Exam: Spring 2023 Time: 1 hour 45 minutes Marks: 30

There are five questions here. Answer all of them

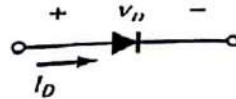1. The Current $I_D = 5 \text{ mA}$ flows through the following diode for $V_D = 0.76 \text{ V}$ at 30° C .




Assuming the ideality factor to be unity and the turn-ON voltage to be 0.75 V at 30° C , calculate


- (a) the reverse saturation current at 30° C . [2]
- (b) the diode current I_D at 343 K temperature for the same value of V_D . [2]
- (c) the diode current I_D at 10° C temperature for the same value of V_D . [2]

Note that V_{ON} and I_s of a diode depend on the system temperature.


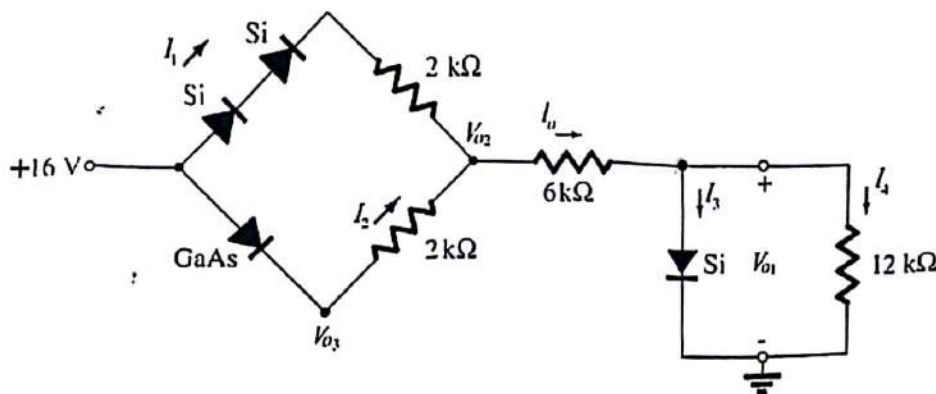
2. Calculate $I_1, I_2, I_3, I_4, I_0, V_{D1}, V_{D2}$ and V_{D3} in the following circuit: [7]



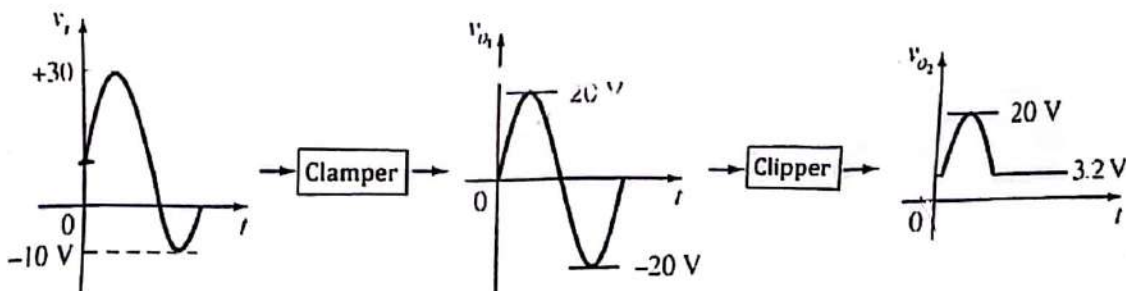
3. Design the clipper and clamper circuit to produce the following output voltage (v_{o2}) according to the given input voltage (v_i). In the following network, the input and output of the clamper circuit are v_i and v_{o1} . For the clipper circuit, the input and output are v_{o1} and v_{o2} . For the clamper circuit, use ideal diodes/diode and for the clipper circuit, use GaAs diode/diodes. [6]



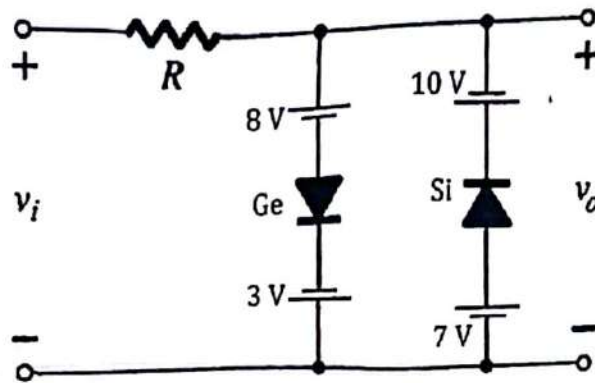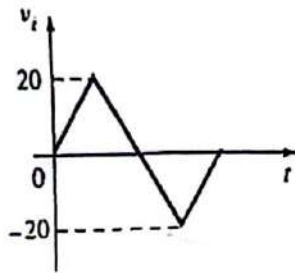4. Sketch the output voltage (v_o) of the following circuit and properly mention the output voltage levels in your sketch. [4]



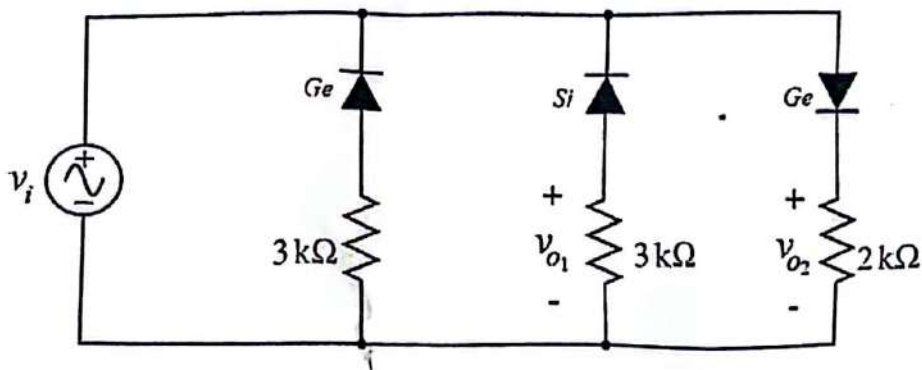5. Consider the input voltage for the following circuit to be a sine wave with an r.m.s value of 10V.



- Draw the v_{o1} and v_{o2} profile from the circuit with proper label values. [2]
- Determine the difference between v_{o1} , v_{o2} and $v_{o1} + v_{o2}$ voltage graphs. [2]
- Determine the average voltage value of v_{o1} . [1]
- Determine the peak inverse voltage of both Si and Ge diodes. [2]