



United International University

Department of Computer Science and Engineering

Course Code: EEE 2113 | Course name: Electrical Circuit

SPRING 2021 | FINAL Examination | 40 marks | 1 hour and 30 minutes

There are four (4) questions here. You have to answer all of them.


Question no - 2 has an option.

Data Generation for example ID - 011xxyyzz

Last 6 digits will be used as data	011	R_{xx}	R_{yy}	R_{zz}
Example ID	011	xx	yy	zz
Your ID	011			


1. Use **Superposition theorem** to find V_o in the following circuit.

10

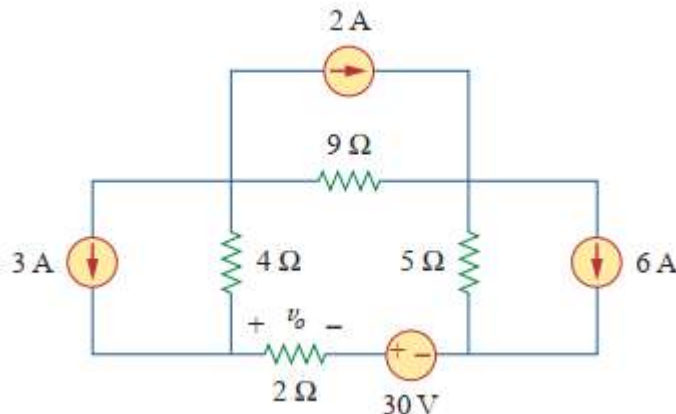


2. Obtain the **Thevenin equivalent** at terminals a-b in the following circuit. Find the **value of R_L** for maximum power absorption. Calculate the amount of **maximum absorbed power** by R_L .

10

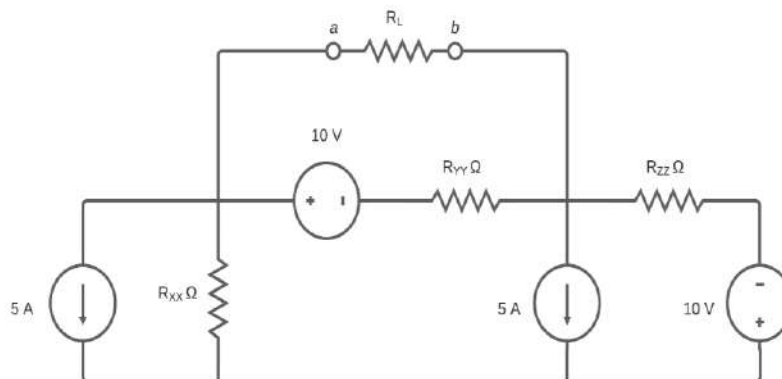


OR

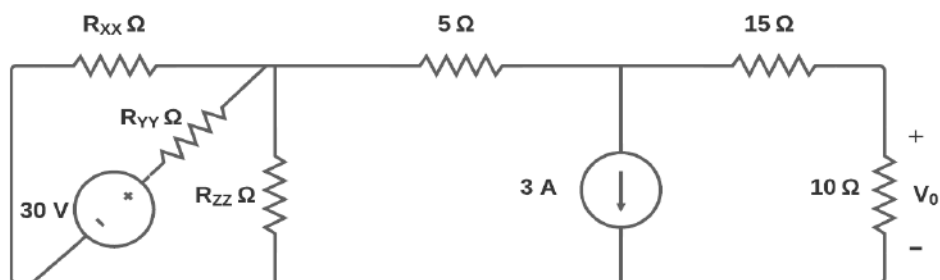
Use **Norton's theorem** to find V_o in the following circuit.



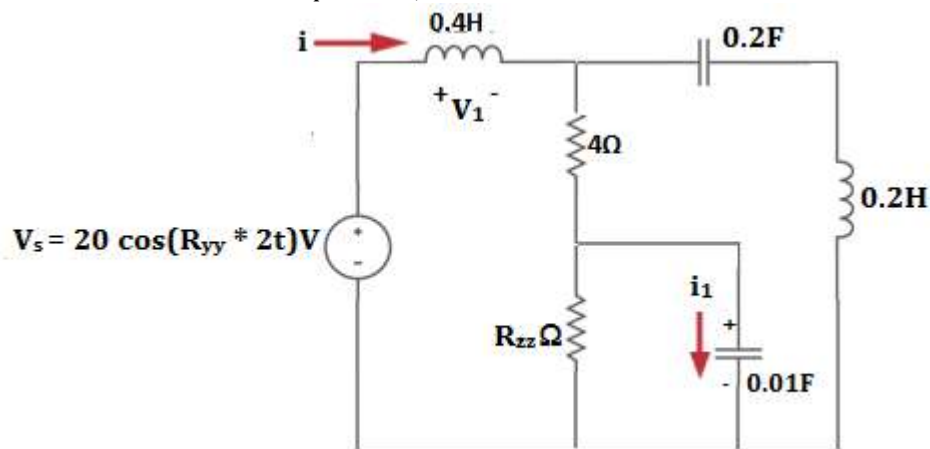3. Find out the value of \mathbf{i} in the following circuit. Also find out the value of $\mathbf{V_1}$ and $\mathbf{i_1}$ using **voltage division rule** and **current division rule**. Represent \mathbf{i} , $\mathbf{V_1}$ and $\mathbf{i_1}$ in time domain.



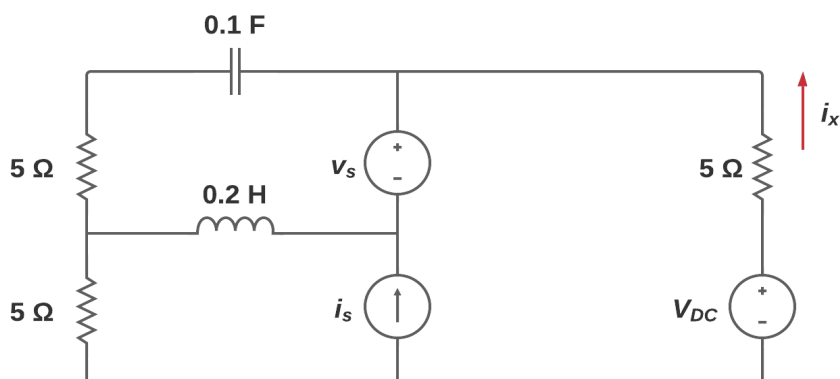4. Using the superposition theorem, find $\mathbf{i_x(t)}$. Here,
 $\mathbf{v_s(t) = 50 \cos(R_{XX} t) V}$
 $\mathbf{i_s(t) = 2 \sin(R_{YY} t) A}$
 $\mathbf{V_{DC} = R_{ZZ} V}$



Any examinee found adopting unfair means will be expelled from the trimester / program as per UIU disciplinary rules

