



United International University (UIU)
Dept. of Computer Science & Engineering (CSE)
Final-Term Exam: Trimester: Summer 2023

Course Code: EEE 2123; Course Title: Electronics
Total Marks: 40; Duration: 2 hours

Any examinee found adopting unfair means would be expelled from the trimester/ program as per UIU disciplinary rules.

There are six(6) questions in this paper. Answer all of them.

Q1(a). For the given NMOS , find the **operating region** in each cases : [4x1=4]

 


Fig 1: Circuit diagram for Q1(a)

- (a) $V_G = 0\text{ V}$, $V_S = -2\text{ V}$, $V_D = 1\text{ V}$, $V_t = 1\text{ V}$
- (b) $V_G = 1.5\text{ V}$, $V_S = 0\text{ V}$, $V_D = 0.1\text{ V}$, $V_t = 1.2\text{ V}$
- (c) $V_G = -2\text{ V}$, $V_S = -3\text{ V}$, $V_D = 5\text{ V}$, $V_t = 1.5\text{ V}$
- (d) $V_G = 5\text{ V}$, $V_S = -1\text{ V}$, $V_D = 5\text{ V}$, $V_t = 1\text{ V}$

Q1(b). The MOSFET shown below has $V_{tn} = 1\text{ V}$, $\mu_n C_{ox} = 0.1\text{ mA/V}^2$. Find the values of **W/L** and **R** so that when $v_I = V_{DD} = +5\text{ V}$, $r_{DS} = 50\ \Omega$ & $v_o = 50\text{ mV}$. [6]

 


Fig 2: Circuit diagram for Q1(b)

Q2. Analyze the circuit below to determine voltages at all nodes and the currents through all branches. Let, $V_{tn} = 1\text{V}$, $k_n'(\text{W/L}) = 1\text{ mA/V}^2$. [6]

 


Fig 3: Circuit diagram for Q2

Q3. Determine the voltage at all nodes and current through all branches for the BJT circuit shown below. Here, $R_E + R_C = 8\text{ k}\Omega$ and $0 < R_E < R_C$ [4]

 


Fig 4: Circuit diagram for Q3

Q4. For the bipolar junction transistor in the following circuit,

$R_B = 100 \text{ k}\Omega$ and $\beta_{\text{forced}} = 15$. Find the value of R_C . Assume silicon diode. [6]

 


Fig 5: Circuit diagram for Q4

Q5(a). . The PMOS network of a random digital system is given below: [4]

 


Fig 6: Circuit diagram for Q5(a)

Draw the corresponding NMOS network using the concept of CMOS technology and mention the expression of the output function, V_{out} .

Q5(b). Implement the following logic function “ f ” in single stage and draw the corresponding circuit diagram: [4]

$$f = (ab + \bar{c})ed + gh$$

Q6. Design an amplifier circuit that can generate the following outputs: [3+3]

(a) $v_0 = 10 v_i - 5 \frac{dvi}{dt}$

(b) $v_0 = 5v_1 + 15v_2$ (here, v_1 and v_2 are two different inputs)

Clearly mention the values of all circuit parameters. Assume that the feedback resistor is $10 \text{ k}\Omega$ in all cases.