



# United International University

Department of Computer Science and Engineering

Course Code: EEE 2113 | Course name: Electrical Circuit

Fall 2020 | FINAL Examination | 25 marks | 90min

There are four (4) questions here. Answer all of them.

## Data Generation for example ID - 011xyyzz

Last 6 digits will be used as data	011	$R_{xx}$	$R_{yy}$	$R_{zz}$
Example ID	011	xx	yy	zz
Your ID	011			

1. Find the value of  $R_L$  in the following circuit for maximum power absorption. Also calculate the amount of maximum absorbed power by  $R_L$ . [6]

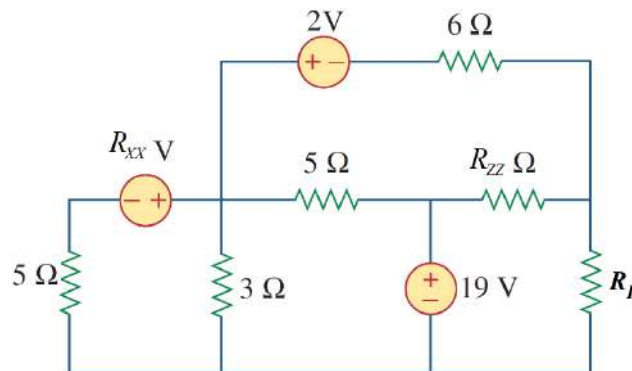


Figure for Q-1

2. Using superposition theorem find current  $i_x(t)$  through  $0.2 H$  inductor. Here, [9]

$$v_s(t) = 10\sin(R_{zz}t + 25^\circ)V$$

$$i_s(t) = 5\cos(R_{yy}t - 5^\circ)V$$

$$V_{DC} = R_{xx} V$$

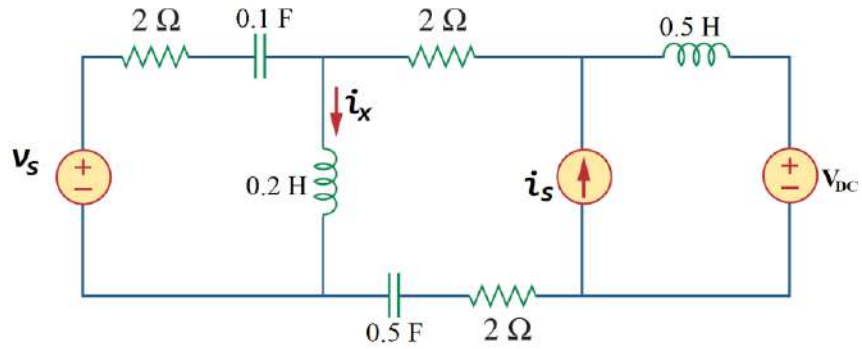


Figure for Q-2

3. Determine  $v_1, v_2, v_3, I, I', I''$  in the following circuit using current and voltage division rules. Also calculate the value of  $L$  in  $H$  and  $C$  in  $F$ . [5]

$$v_s(t) = 75\cos(R_{xx} \times 5t) \text{ V}$$

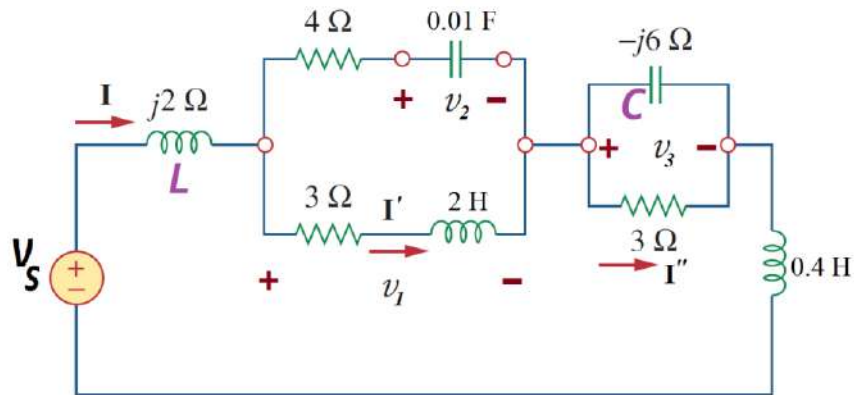


Figure for Q-3

4. Use mesh analysis method to obtain mesh currents in the following circuit. You must show detail of all calculations. [5]

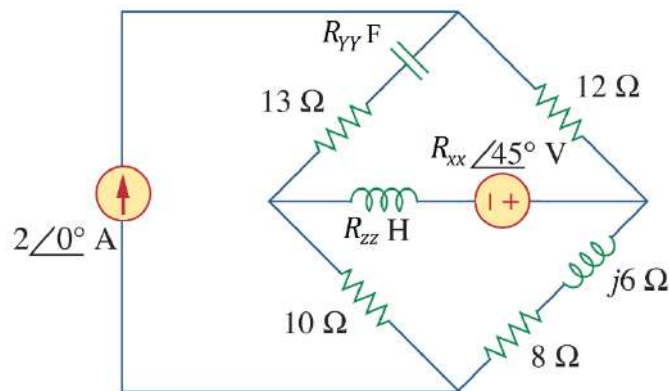


Figure for Q-4

**Any examinee found adopting unfair means will be expelled from the trimester / program as per UIU disciplinary rules**