




United International University (UIU)  
Dept. of Computer Science & Engineering (CSE)  
**Final-Term Exam: Trimester: Fall 2023**

Course Code: EEE 2123; Course Title: Electronics  
Total Marks: 40; Duration: 2 hours

Any examinee found adopting unfair means would be expelled from the trimester/ program as per UIU disciplinary rules.

There are six(6) questions in this paper. Answer all of them.

 
**Q1(a).** For the given NMOS with  $V_t = 1\text{V}$ , find the **operating region** in each cases :  
[5x1=5]



Case	$V_s$	$V_g$	$V_d$
a	+1.0	+1.0	+2.0
b	+1.0	+2.5	+2.0
c	+1.0	+2.5	+1.5
d	+1.0	+1.5	0
e	0	+2.5	1.0


*Fig 1: Circuit diagram and data table for Q1(a)*

**Q1(b).** Determine the values of  $R_D$  and  $R_S$ , so that the transistor operates at  $I_D = 0.3\text{mA}$  and  $V_D = +0.4\text{V}$ . The NMOS transistor has  $V_t = 1\text{V}$ ,  $\mu_n C_{ox} = 60\text{ }\mu\text{A/V}^2$ ,  $W/L = 40$  [6]

 

*Fig 2: Circuit diagram for Q1(b)*


**Q2.** Analyze the circuit below to determine voltages at all nodes and the currents through all branches. Let,  $V_{tn} = 1V$ ,  $k_n'(W/L) = 1 \text{ mA/V}^2$ . [6]

 

**Fig 3: Circuit diagram for Q2**


**Q3.** The transistor shown below is operating at the edge of saturation. Find the values of voltages at all nodes ( $V_B$ ,  $V_C$ ,  $V_E$ ) and the currents through all branches.

Here,  $\beta = 100$ . [4]

 


**Fig 4: Circuit diagram for Q3**

**Q4.** For the transistor in the following circuit,  $\beta = 50$  and  $\beta_{\text{forced}} = 15$ . Analyze the circuit to the value of voltage at all nodes and current through all branches.[5]

 

**Fig 5: Circuit diagram for Q4**

**Q5(a).** The PMOS network of a random digital system is given below: [4]

 

**Fig 6: Circuit diagram for Q5(a)**

Draw the corresponding NMOS network using the concept of CMOS technology and mention the expression of the output function,  $V_{\text{out}}$ .

**Q5(b).** Implement the following logic function “ f ” in single stage and draw the corresponding circuit diagram: [4]

$$f = A\bar{B} + B(\bar{C} + \overline{CD})$$

**Q6.** Design an amplifier circuit that can generate the following outputs: [3+3]

(a)  $v_0 = 5 \int v_i dt + 15 v_i$

(b)  $v_0 = v_1 + \frac{1}{3} \frac{dv_2}{dt} - v_3$  (Here  $v_1$ ,  $v_2$  and  $v_3$  are three different inputs)

Clearly mention the values of all circuit parameters. Assume that the feedback resistor is 1 k $\Omega$  in all cases.