



United International University (UIU)
Dept. of Computer Science & Engineering (CSE)
Mid-Term Exam: Trimester: Summer 2023

Course Code: EEE 2113; Course Title: Electrical Circuits
Total Marks: 30; Duration: 1 hour 45 minutes

Any examinee found adopting unfair means would be expelled from the trimester/ program as per UIU disciplinary rules.

Question 1: Answer all the questions.

(6 Marks)

The charge flowing in a wire having $20\ \Omega$ resistance is shown in **Figure 1**. Answer the following questions: [4+2]

- Clearly** sketch the corresponding current and find current at $t = 2.5$ sec and $t = 5.5$ sec.
- Determine** the time when maximum power is delivered to the element. Also, **find** the maximum power.

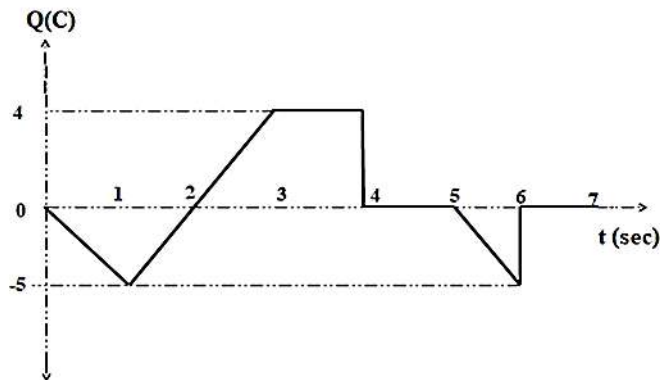


Figure 1.

Question 2: Answer all the questions.

(6 Marks)

For the circuit shown in **Figure 2**, determine the following questions: [3+3]

- Find the equivalent resistance across the terminals **a-b**.
- A **30 V** voltage source is connected to the terminals **a-b**, the **positive** terminal of the source is connected to **a** and the **negative** terminal is connected to **b**. Find the currents I_{ce} and I_{eb} using **current division rule**.

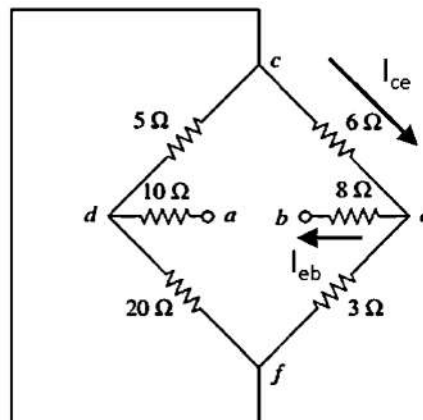
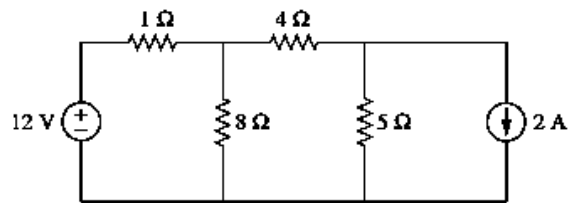


Figure 2.

Question 3: Answer all the questions**(6 Marks)**

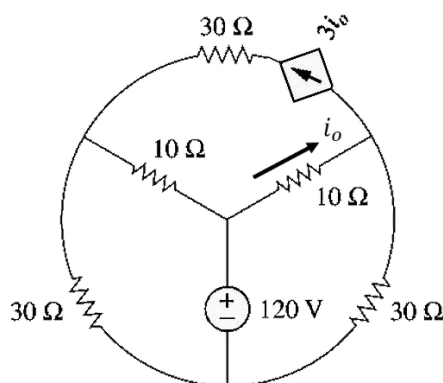
[6]

**Figure 3.**

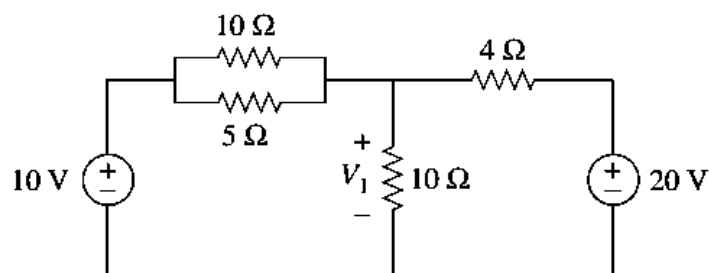
Use Kirchoff's Current Law (**KCL**) and Kirchoff's Voltage Law (**KVL**) to find **all the branch currents and node voltages** of the above circuit in **Figure 3**.

Question 4: Answer all the questions.**(6 Marks)**

For the circuit shown in **Figure 4**, determine i_o and current through the battery using **mesh** [3+3] **analysis**.

**Figure 4.****Question 5: Answer all the questions.****(6 Marks)**

[3+3]

**Figure 5.**

For the circuit shown in **Figure 5**, answer the followings using **node analysis**:

- Determine** the current through the 5Ω resistor and V_1 .
- Evaluate** which voltage source is supplying power to the circuit.