



United International University (UIU)  
Dept. of Computer Science & Engineering (CSE)  
**MID Exam, Trimester: Spring 2024**

Course Code: CSE 113/EEE 2113; Course Title: Electrical Circuits

Total Marks: 30; Duration: 1 hour 30 min

Any examinee found adopting unfair means would be expelled from the trimester/ program as per UIU disciplinary rules.

**Question 1: Answer all the questions.**

**(8 Marks)**

Answer the following questions for the circuit shown in **Figure 1**:

[4+4]

- The current shown in **Figure 1** is flowing through a  $5\Omega$  wire. Now, draw the charge,  $q$  vs. time graph for this current considering the initial charge in the wire is  $1C$  at  $t=0s$ .
- Draw the power absorbed by this wire vs. time graph.

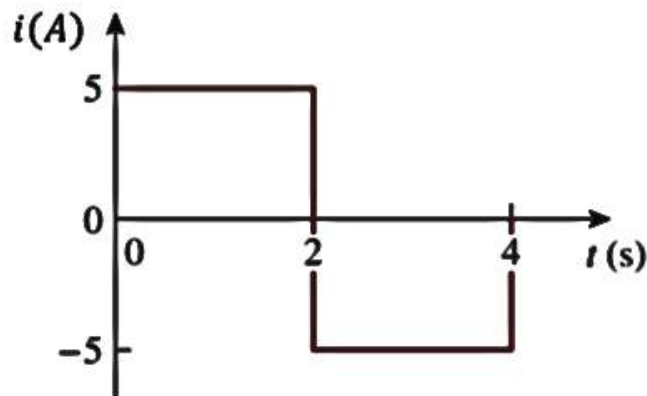


Figure 1

**Question 2: Answer all the questions.**

**(6 Marks)**

For the circuit shown in **Figure 2**, answer the following questions:

[3+3]

- Write the KVL equations for the Loops,  $L1$  and  $L2$ .
- Calculate the values of  $V_x$  and  $I_y$ .

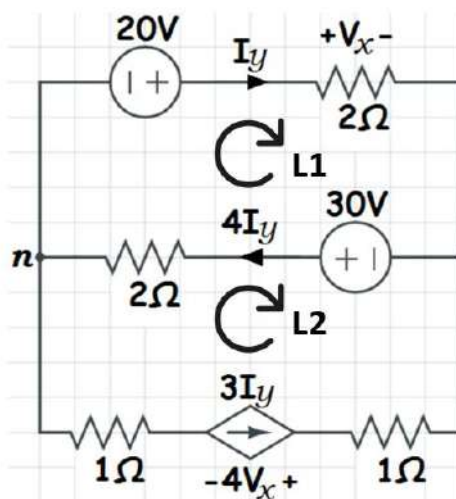
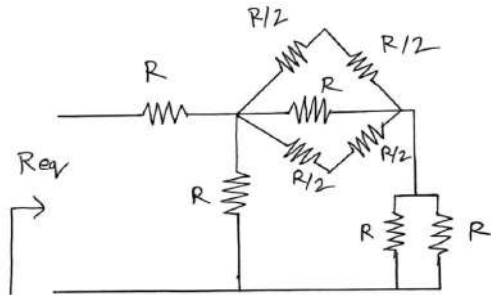
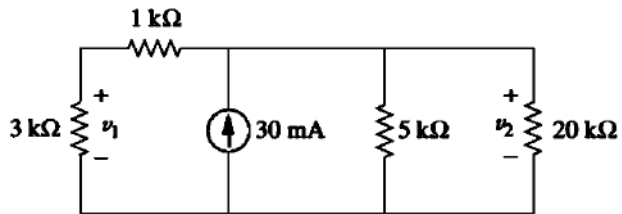


Figure 2.

**Question 3: Answer all the questions****(8 Marks)**Answer the following questions for the circuit shown in **Figure 3 (a-b)**:



[4+4]

- If  $R_{eq} = 10\ \Omega$  for the circuit shown in **Figure 3(a)**, then find the value of  $R$ .
- Figure out the values of  $v_1$ ,  $v_2$  in the circuit shown in **Figure 3(b)**.

**Figure 3a****Figure 3b****Question 4: Answer all the questions.****(8 Marks)**Answer the following questions for the circuit shown in **Figure 4 (a-b)**:

[4+4]

- Find the current,  $i$ , and the voltage,  $V_o$  in **Figure 4a** using mesh analysis.
- Using nodal analysis in **Figure 4b**, find the values of  $v_1$  and  $v_2$ .

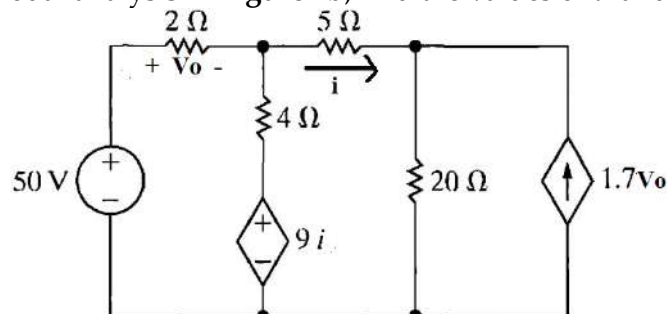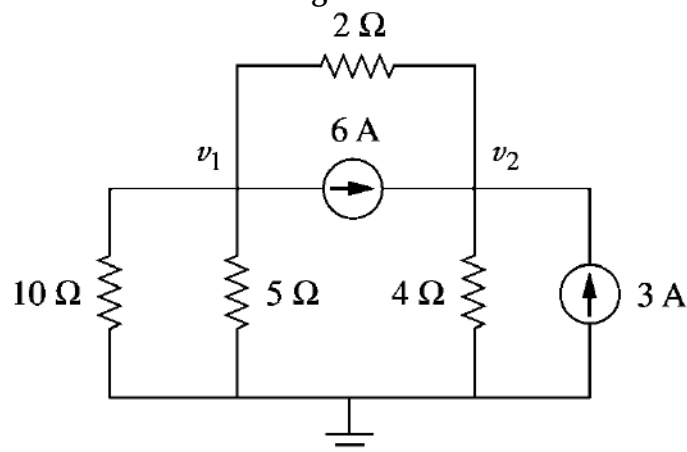**Figure 4a.****Figure 4b.**