

Any examinee found adopting unfair means would be expelled from the trimester/ program as per UIU disciplinary rules.

Q1. I/V characteristics of a diode operating at a fixed temperature is given below. [3+2+2]

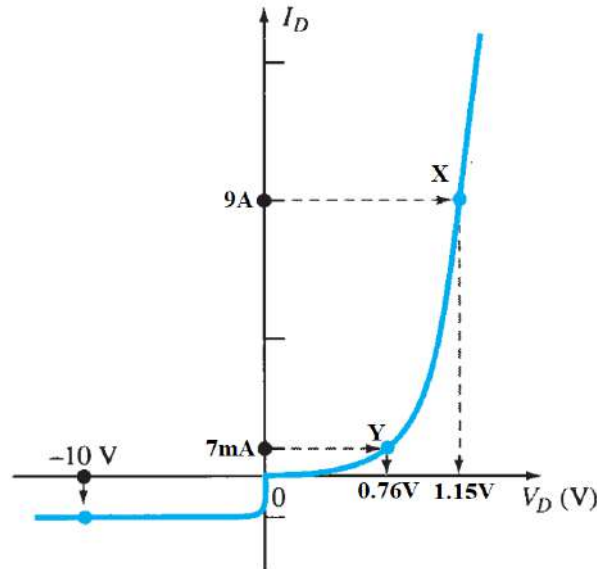


Fig 1: Diagram for Q1

Determine the followings:

- The operating temperature (for $n = 2$). [Hint: Use $I_D = I_S (e^{\frac{V_D}{nV_T}})$]
- Reverse saturation current at that temperature.
- Draw the approximate I/V curve for a different operating temperature of 50°C with reference to the given I/V curve.

Q2. For the following circuit :

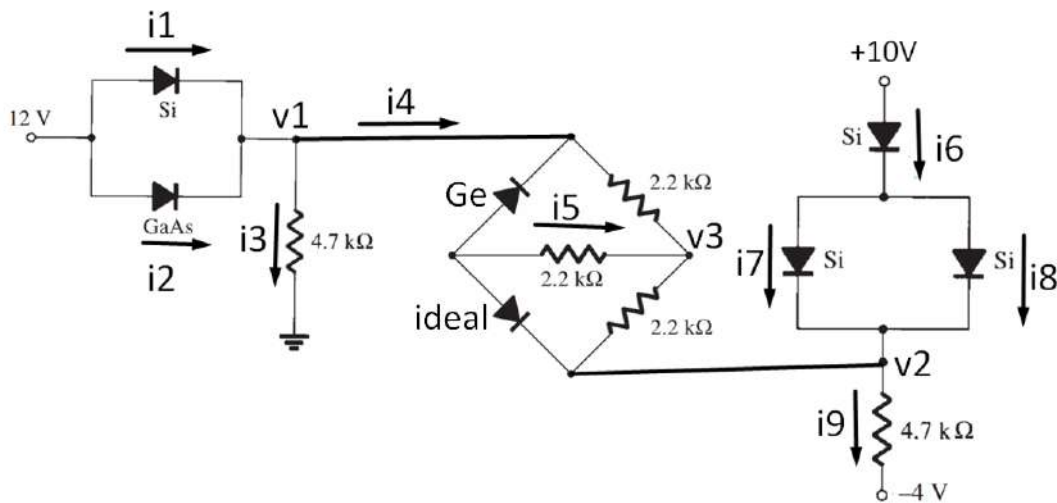


Fig 2: Circuit diagram for Q2

Draw the simplified diagram and hence find the values of $i_1, i_2, i_3, i_4, i_5, i_6, i_7, i_8, i_9$ and v_1, v_2, v_3 . [8]

Q3.

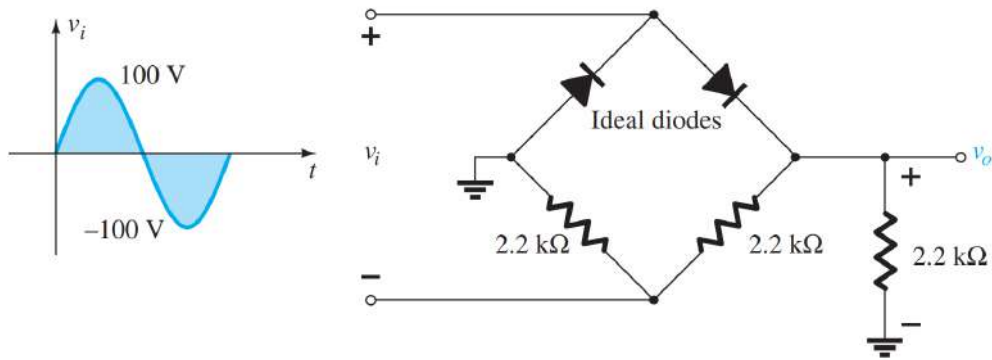


Fig 3: Circuit diagram for Q3

- Express v_o in terms of v_i . [2]
- Find the maximum value and average value of v_o . [2]
- Sketch v_o and v_i in the same plot mentioning peak values. [2]
- Calculate PIV of any diode given in the above network. [1]

Q4. Sketch i_R and v_o for the network of following circuit for the input shown below: [4]

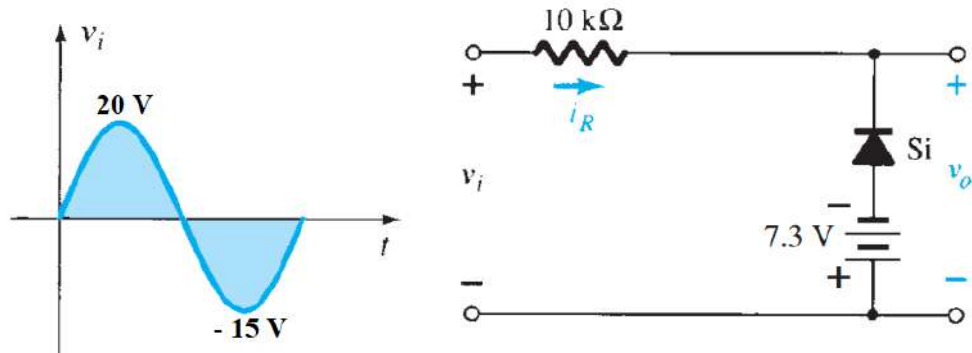


Fig 4: Circuit diagram for Q4

Q5. Design a clamper to perform the function indicated in following figure(Fig 5): [4]

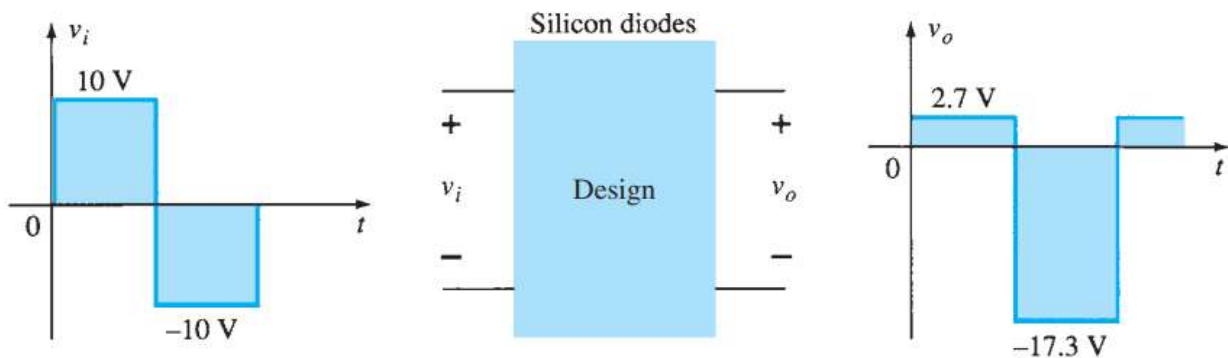


Fig 5: Diagram for Q5