



United International University  
Department of CSE  
CSE 2113: Electrical Circuits  
Final Examination  
Fall 2022

Time: 2 Hours Full Marks: 40

1.

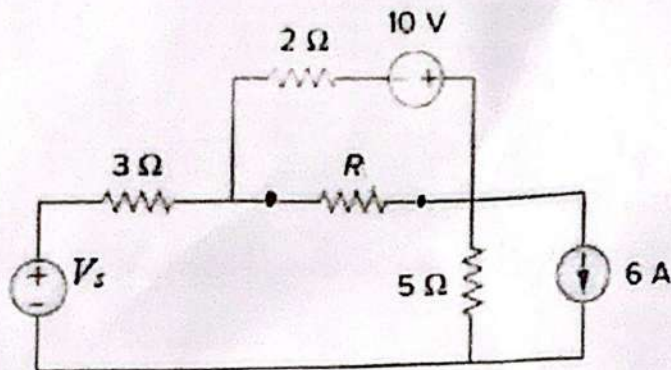


Figure 1 for Question 1.

- (a) Find the value of  $R$  that would result in the maximum power absorbed by that resistor. Assume that  $V_s = 22\text{ V}$ . [7]
- (b) Find the maximum power delivered to the resistor  $R$ . [2]

2.

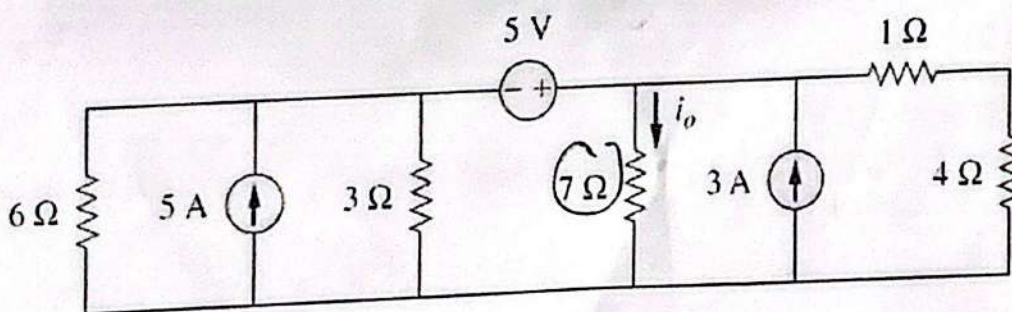


Figure 2 for Question 2.

For the above circuit shown in Figure 2, determine the power absorbed the in  $7\Omega$  resistor using Source transformation. [8]



3

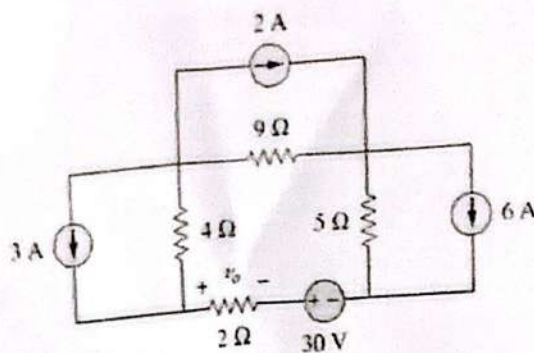


Figure 3 for Question 3.

For the above circuit shown in Figure 3, determine  $v_o$  using Superposition. [8]

4.

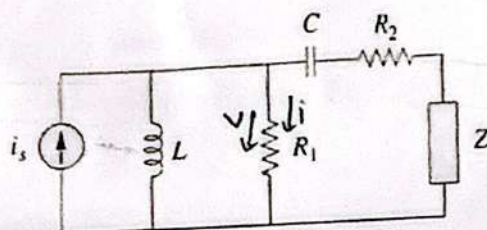


Figure 4 for Question 4.

For the above circuit shown in Figure 4, the following information is given:  $i_s = 5 \sin(277t + 40^\circ)$ ,  $L = 10\text{mH}$ ,  $R_1 = 100\Omega$ ,  $R_2 = 20\Omega$ ,  $C = 100\mu\text{F}$ ,  $v_{R_1} = 14.46 \sin(277t + 125.2^\circ)$ . Now, determine the followings:

- Power absorbed by  $R_1$ . [2]
- Value of  $Z$ . Explain what type of electrical component constitutes the impedance,  $Z$ . [4]
- Voltage across  $R_2$  resistor. [2]
- Determine the phase angle difference between  $i_s$  &  $v_{R_2}$ . Explain which one is leading. [2]

5.

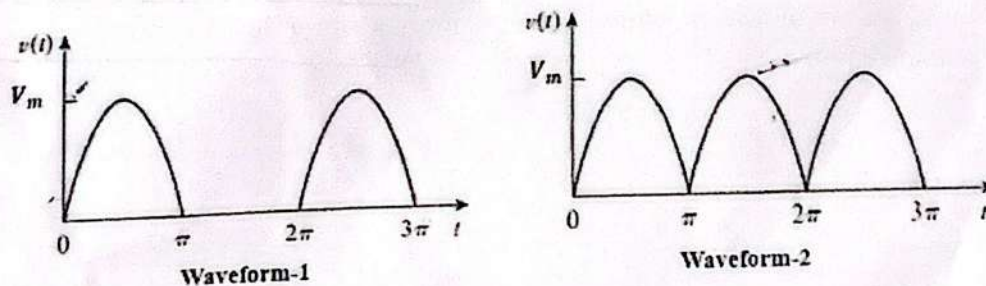


Figure 5 for Question 5.

When the voltage shown in waveform-1 is applied across a  $10\Omega$  resistor, on average 2.5W power is absorbed by the resistor. If the voltage shown in waveform-2 is applied across the same resistor, then determine the average absorbed power. [5]