



United International University (UIU)
Dept. of Computer Science & Engineering (CSE)
Final Exam: Trimester: Summer 2023

Course Code: EEE 2113; Course Title: Electrical Circuits
Total Marks: 40; Duration: 2 hours

Any examinee found adopting unfair means would be expelled from the trimester/ program as per UIU disciplinary rules.

Question 1: Answer all the questions.

(10 Marks)

For the above circuit shown in **Figure 1**, determine I_o using Superposition and the power dissipated in 15Ω resistance. [8+2]

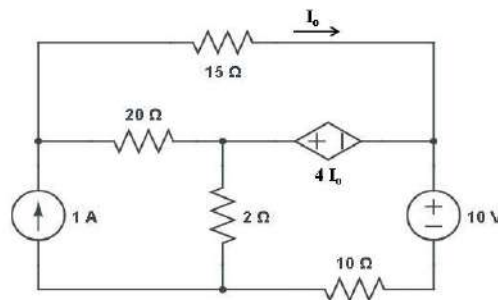


Figure 1.

Question 2: Answer all the questions.

(10 Marks)

For the circuit shown in **Figure 2**, determine the following questions: [5+3

- i) For the circuit shown below, find the thevenin equivalent circuit at the **A-B** terminal. +2]
- ii) For any resistance connected right to **A-B** terminal, what will be the maximum power delivered to the resistance?
- iii) If 10Ω resistance is connected between **A-B**, then would maximum power be achieved? If not then what should you do?

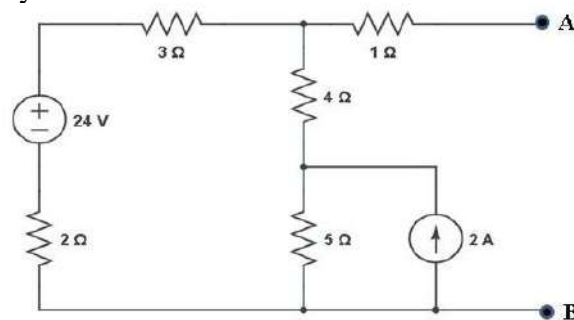


Figure 2.

Question 3: Answer all the questions

(10 Marks)

For the circuit shown in **Figure 3**, $V_s(t) = 15 \cos(100t + 30^\circ)$. Now, determine the following questions: [6+4]

- (a) Find equivalent impedance at terminals a – b.
- (b) Find $I_1(t)$, $V_c(t)$, $V_d(t)$ and $V_{cd}(t)$.

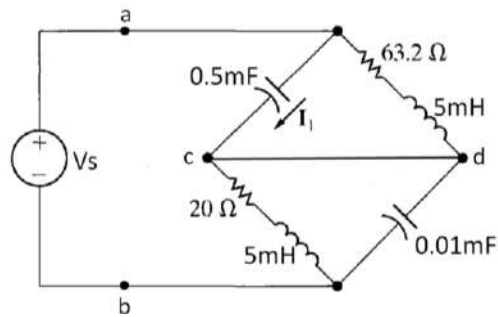


Figure 3.

Question 4: Answer all the questions.

(10 Marks)

For the waveform shown in **Figure 4a**, determine the rms value of the current, i_{rms} . Also, [5+5]
determine the power absorbed by 5Ω resistance for the circuit shown in **Figure 4b**.

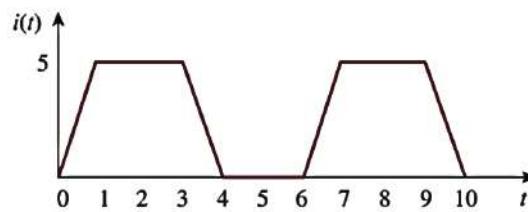


Figure 4a.

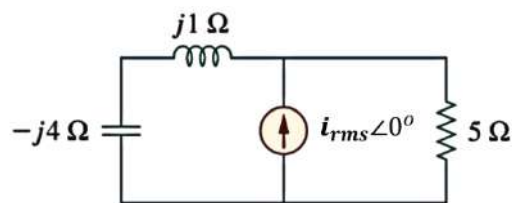


Figure 4b.